

Example:1. Circuit to state diagram

Present states:

A and B

Input:


DA, DB, x

Next states:

$A^+$  and  $B^+$

Output:

y

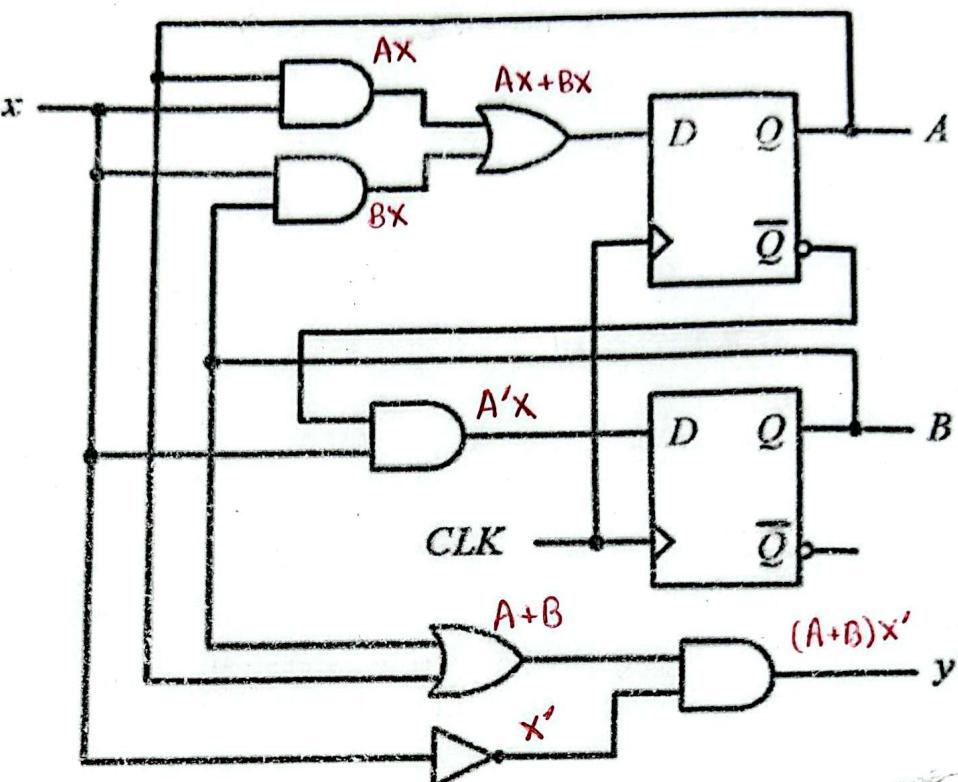

$$DA = Ax + Bx'$$

$$DB = A'x$$

$$y = (A+B)x'$$

	A	B	x	DA	DB	y
0	0	0	0	0	0	0
0	1	0	0	1	0	0
1	0	0	1	0	1	0
0	0	1	0	0	0	0
0	1	0	1	1	0	1
1	0	1	0	0	1	0
1	1	1	1	1	1	1

A	B	X	D	A	DB	Y	$A^+$	$B^+$
0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1	1
0	1	0	0	0	1	0	0	0
0	1	1	1	1	0	1	1	1
1	0	0	0	0	1	0	0	0
1	0	1	1	0	0	1	0	0
1	1	0	0	0	1	0	0	0
1	1	1	1	0	0	1	0	0

D - Flip - Flop

D	S
0	0
0	1
1	1

A	B	X	$A^+$	$B^+$	Y
0	0	0	0	0	0
0	0	1	0	1	$x'g + xA \oplus Aq$
0	1	0	0	0	$x'A + gq$
1	0	0	1	0	$x(g + A) = qr$
0	1	1	0	0	1
1	0	1	1	0	0
1	1	0	1	0	0
1	1	1	1	1	0

$$D \oplus A = A^+$$


$$D \oplus B = B^+$$

$2^n$  states

n flip-flop  
 $2^n$  states


2 flip-flop

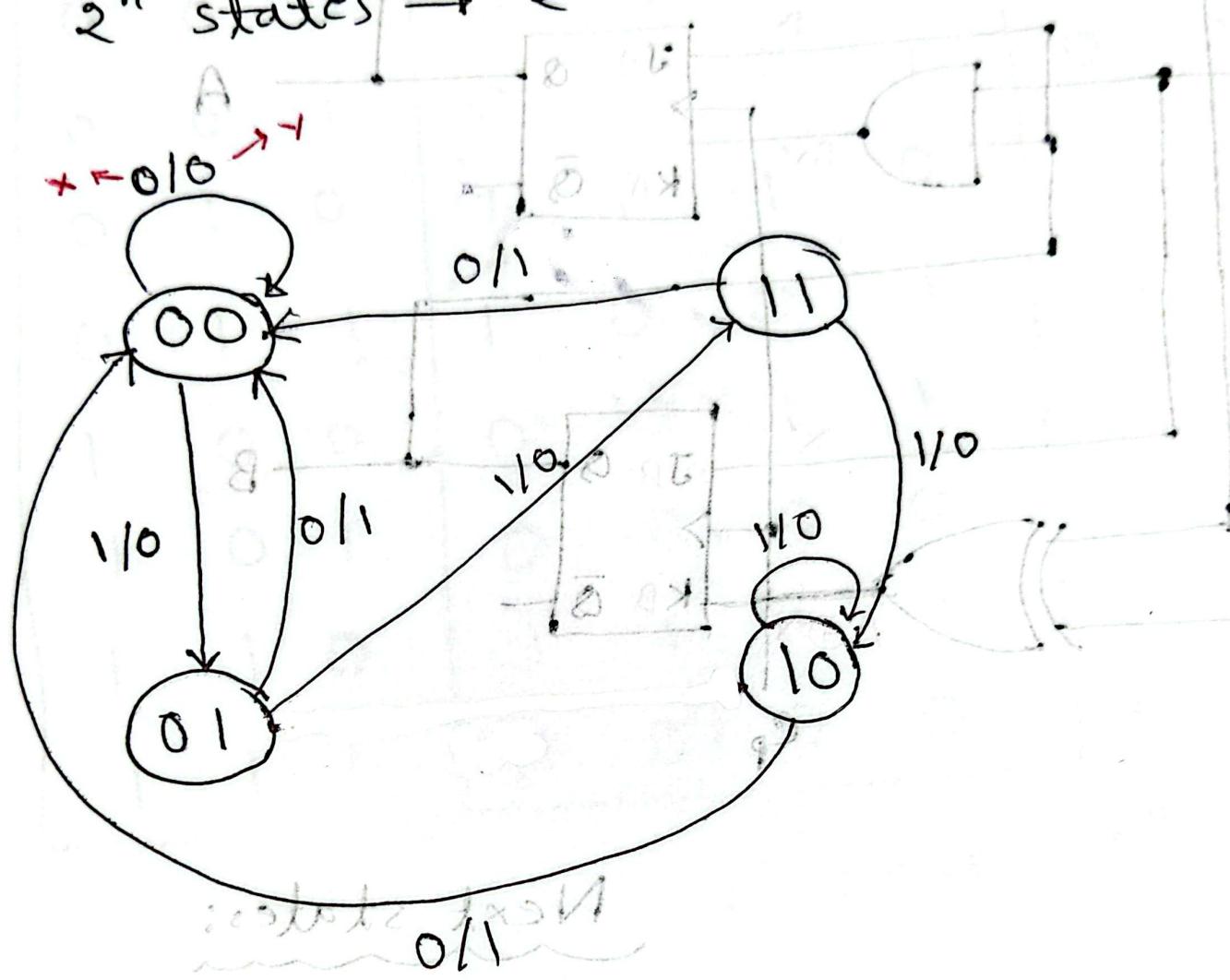$2^n$  states  $\rightarrow 2^2 \rightarrow 4$  states



State Diagram

### Ex-2:

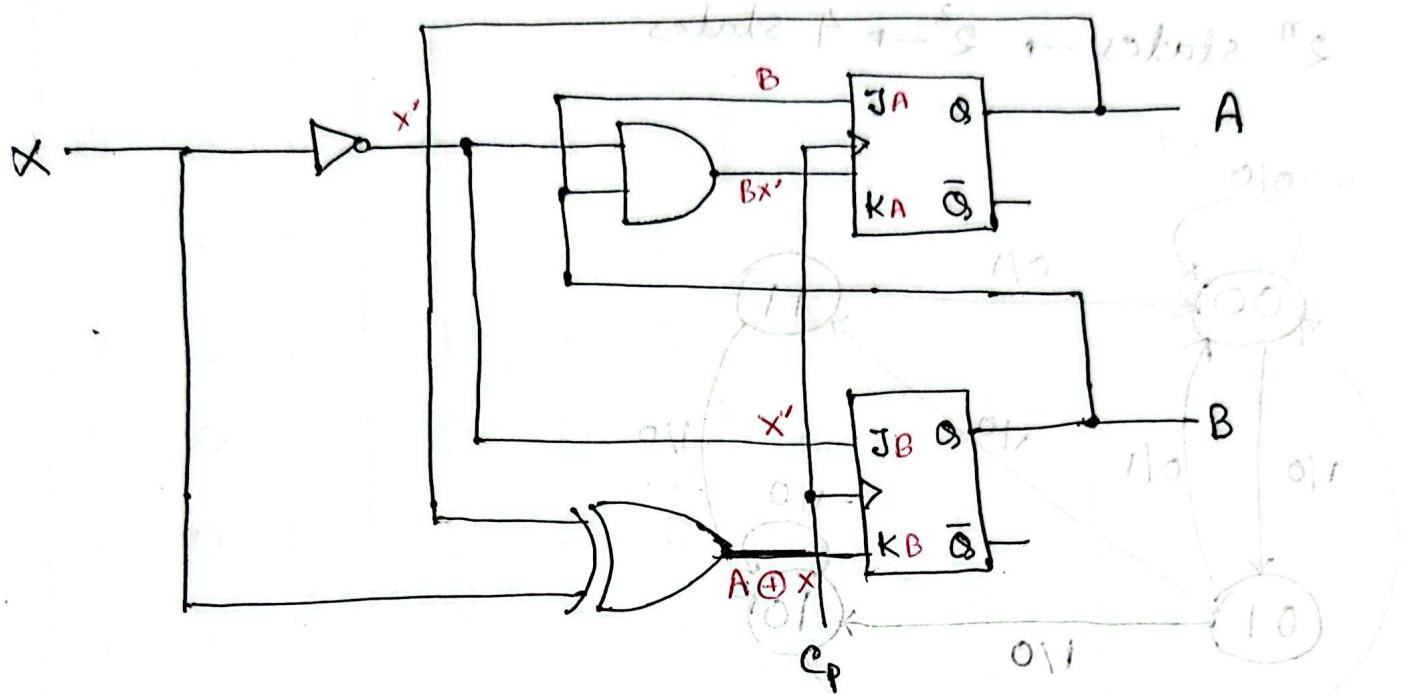

## Present states:

A, B

Next states:

$A^+$ ,  $B^+$

Input:

JA, KA, JB, KB, X

XOR

Hence,  $JA = B$

$$JB = X'$$

$$KA = BX'$$

$$KB = A \text{ XOR } X$$

(No output given)

$$KB = A \oplus X$$


X                    X                    X

A	B	X	JA	KA	JB	KB	A +	B +
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	1
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	0	0
1	1	0	1	1	1	1	0	1
1	1	1	1	0	0	0	1	1

$2 \text{ ff} , 2^n = 2^2 = 4 \text{ states}$

### J-K Flip-Flop


J	K	Q	Q'
0	0	No change	
0	1	0	1
1	0	1	0
1	1	Toggle	

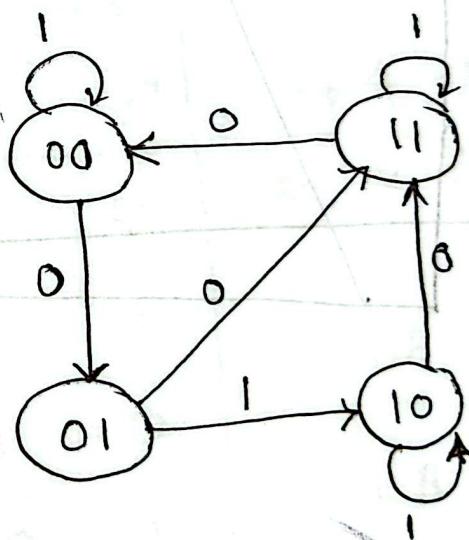

state Diagram

State Diagram to circuit Diagram Solutions 47-48

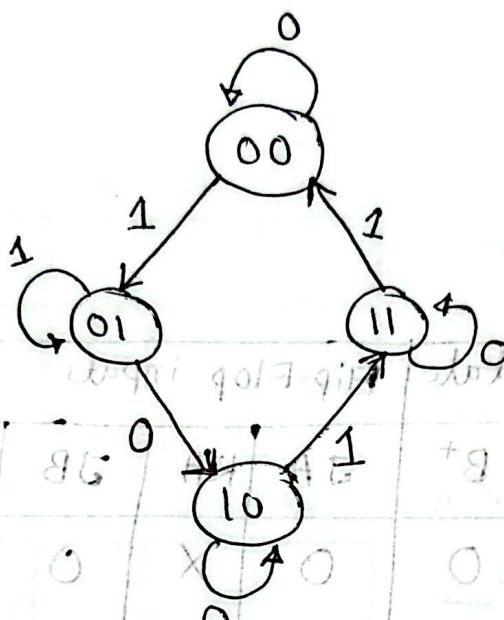Ex-1: Given state Diagram as follows, get the sequential circuit using J-K flip-flop.



J-K flip-flop

0 1

0 X

X X

log<sub>2</sub><sup>m</sup> states

log<sub>2</sub><sup>m</sup> states

m flip-flop A

0 0

1 0

0 1

1 1

→ 4 states

so, 2 flip-flop

0 0

1 0

0 1

1 1

JA JB

KA KB

0 0

1 0

0 1

1 1

0 0

1 1

0 0

1 1

0 0

1 1

0 0


1 1

0 0

&lt;p

J-K ff excitation table:


$S$	$S^+$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

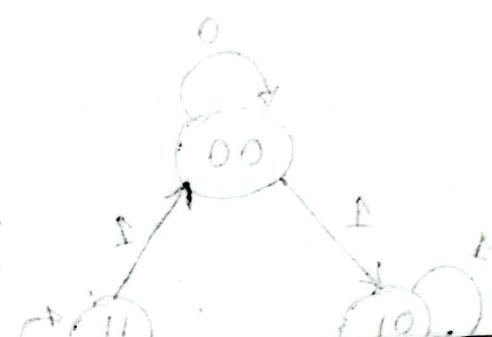

Present state	Input	Next state		Flip-Flop inputs			
		$A^+$	$B^+$	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	X	0	X
0	0	1	0	0	X	1	X
0	1	0	1	0	X	X	1
0	1	1	0	1	X	X	0
1	0	0	1	0	X	0	X
1	0	1	0	0	X	0	0
1	1	1	1	1	X	0	0
1	1	0	0	0	X	1	X
1	1	1	0	0	X	0	0
1	1	0	1	1	X	1	0
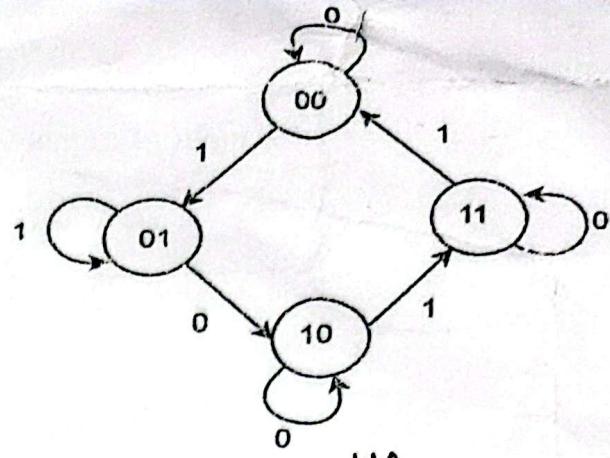
# State to circuit diagram

Following the table,  
we're doing k-MAP's  
for JA, KA, JB, KB.



		00	01	11	10	JA	
		Bx	B'x'	B'x	Bx	Bx'	
A		A'	0	1	3	2	1
0	A'	X <sub>4</sub>	X <sub>5</sub>	X <sub>7</sub>	X <sub>6</sub>		
1	A						

		00	01	11	10	KA	
		Bx	B'x'	B'x	Bx	Bx'	
A		A'	X <sub>0</sub>	X <sub>1</sub>	X <sub>3</sub>	X <sub>2</sub>	
0	A'						
1	A						

		00	01	11	10	JB	
		Bx	B'x'	B'x	Bx	Bx'	
A		A'	0	1	X <sub>3</sub>	X <sub>2</sub>	
0	A'						
1	A	4	1	5	X <sub>7</sub>	X <sub>6</sub>	

		00	01	11	10	KB	
		Bx	B'x'	B'x	Bx	Bx'	
A		A'	X <sub>0</sub>	X <sub>1</sub>	1	2	
0	A'						
1	A	X <sub>4</sub>	X <sub>5</sub>	1	7	6	

$$\begin{aligned}
 &= A + A'x' \\
 &= (A \oplus x)
 \end{aligned}$$


From hence,

$$\therefore JA = Bx'$$

$$\therefore KA = Bx$$

$$\therefore JB = x$$

$$\therefore KB = (A \oplus x)'$$

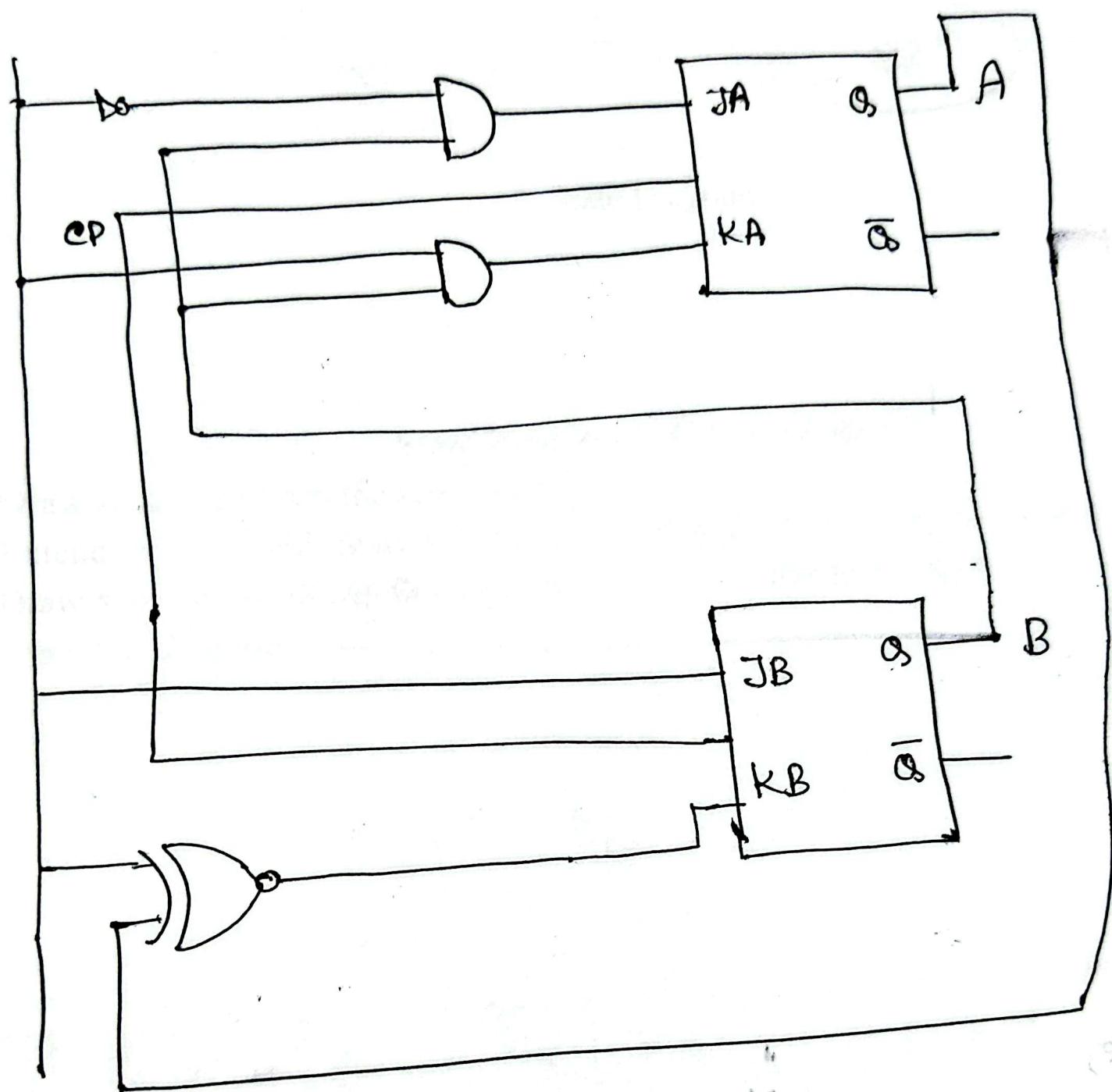

Circuit Diagram

AG  
AK

Ex-2:

Using D-ff find circuit diagram  $\rightarrow$

Present state	Input	Next state	Output	DA	DB		
A	B	X	A <sup>+</sup>	B <sup>+</sup>	Y	DA	DB
0	0	0	0	0	0	0	0
0	0	1	0	1	1	0	1
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
1	0	0	1	0	0	1	0
1	0	1	1	1	1	1	1
1	1	0	0	1	0	1	1
1	1	1	0	0	0	0	0

D-ff excitation table

A	Bx	B'x'	B'x	Bx	Bx'
A'	0	1	3	2	1
A	1	1	5	7	6

A	Bx	B'x'	B'x	Bx	Bx'
A'	0	1	3	2	1
A	0	0	1	1	0

A	Bx	B'x'	B'x	Bx	Bx'
A'	0	1	3	2	1
A	1	1	5	7	6

$$DA = AB' + Bx'$$


A	Bx	B'x'	B'x	Bx	Bx'
A'	0	1	3	2	1
A	0	1	5	7	6

$$Y = B'x$$

$$DA = AB' + Bx'$$

$$DB = A'x + B'x + ABx'$$

$$Y = B'x$$

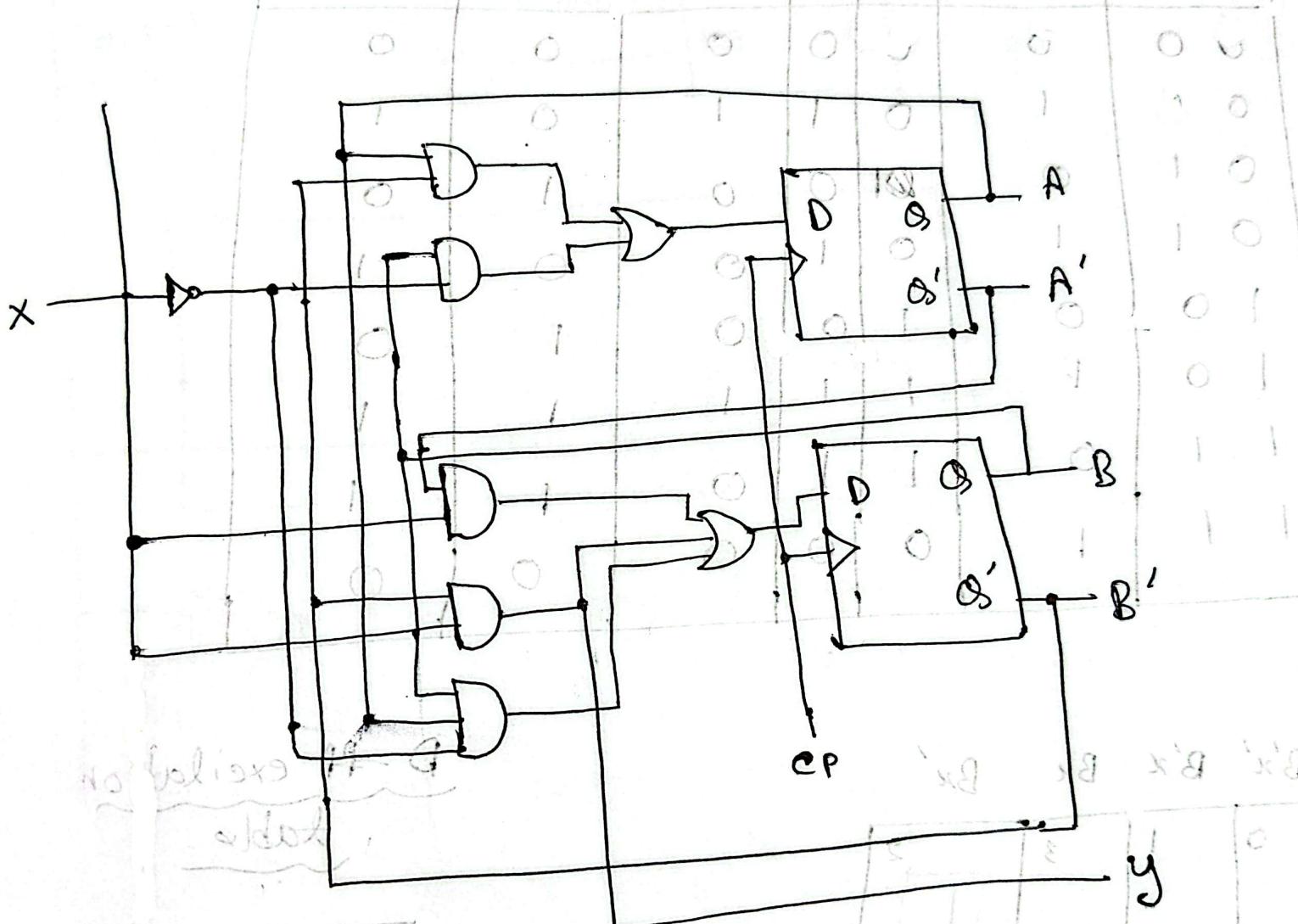

$$AB + BA = AB$$


## Counter Design

Synchronous (Parallel Counters):



- \* Design a 2-bit synchronous binary counter  
(Using T-ff)

$$m = 2$$
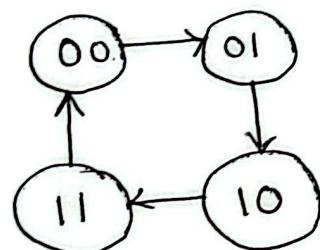
$$\text{states} \rightarrow 2^m = 2^2 = 4$$



Present state	Next state	T & f inputs
A <sub>1</sub> , A <sub>0</sub>	A <sub>1</sub> <sup>+</sup> , A <sub>0</sub> <sup>+</sup>	TA <sub>1</sub> , TA <sub>0</sub>
0 0	0 1	0 1
0 1	1 0	1 1
1 0	1 1	0 1
1 1	0 0	1 1

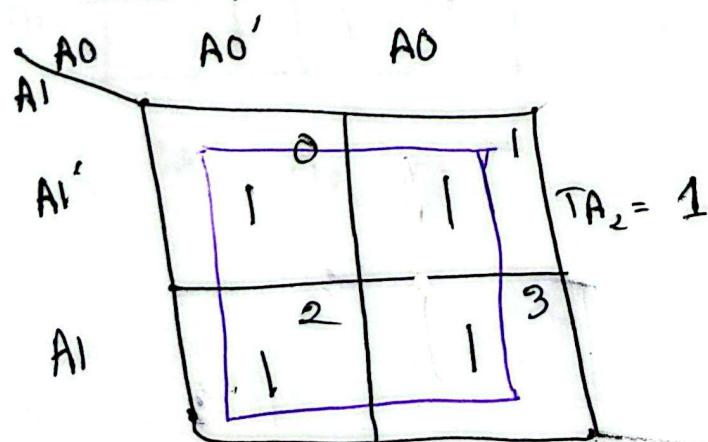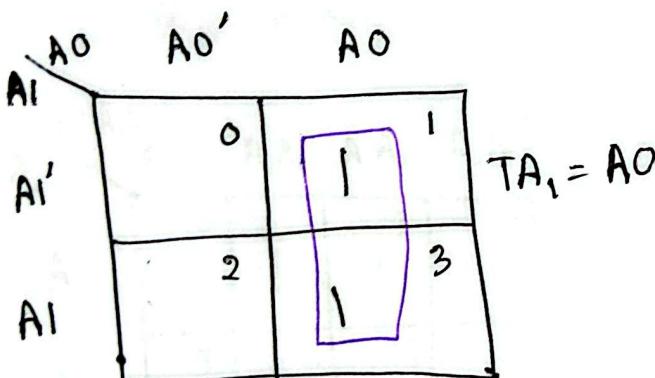


Q <sub>n</sub>	Q <sub>n+1</sub>	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table of T-ff


Measured values

: (constant load) over one

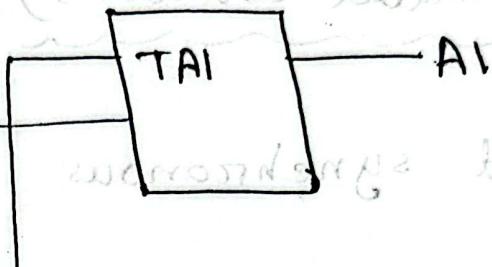

reference period second stage kid-S is refi-


(42 - T<sub>refi</sub>)

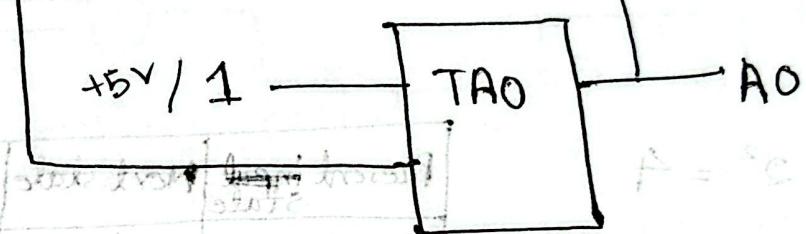

AT <sub>1</sub> , AT <sub>2</sub>	TA <sub>1</sub> , A <sub>1</sub>	A <sub>1</sub> , A <sub>2</sub>
1 0	1 0	0 0
1 1	0 1	1 0
0 0	1 1	0 1

$$TA_1 = A_0$$

$$TA_0 = 1$$

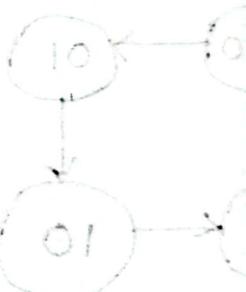




AT <sub>1</sub>	AT <sub>2</sub>	AT <sub>3</sub>
0	0	0
1	1	0

$$OA = AT$$


AT <sub>1</sub>	AT <sub>2</sub>	AT <sub>3</sub>
0	0	1
1	1	1

OA

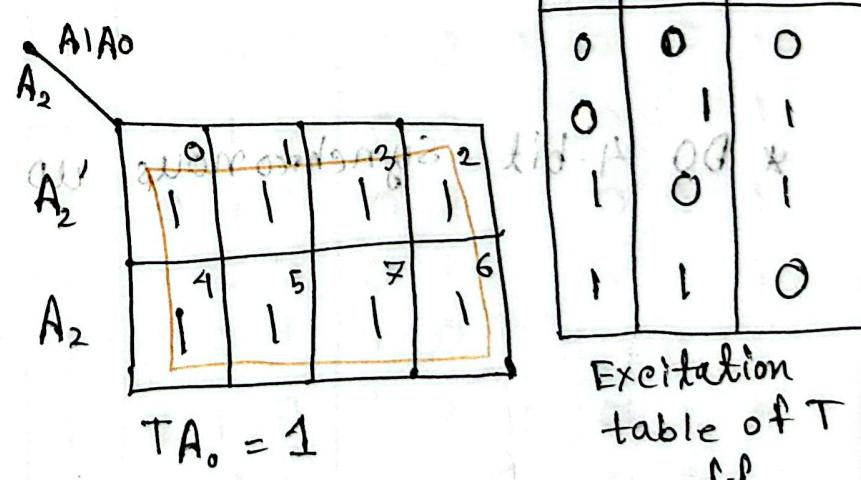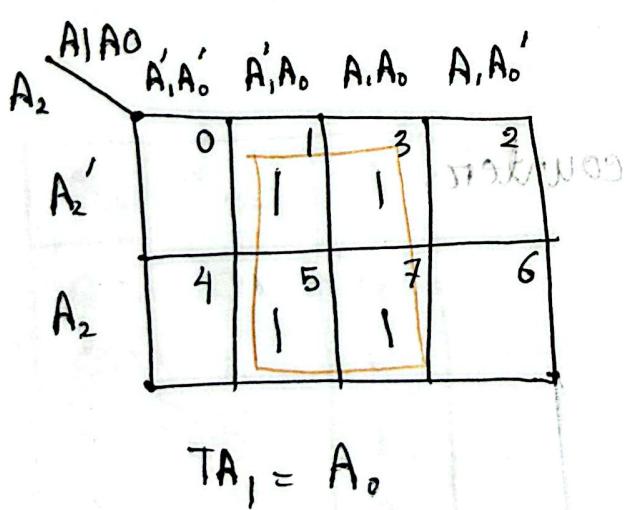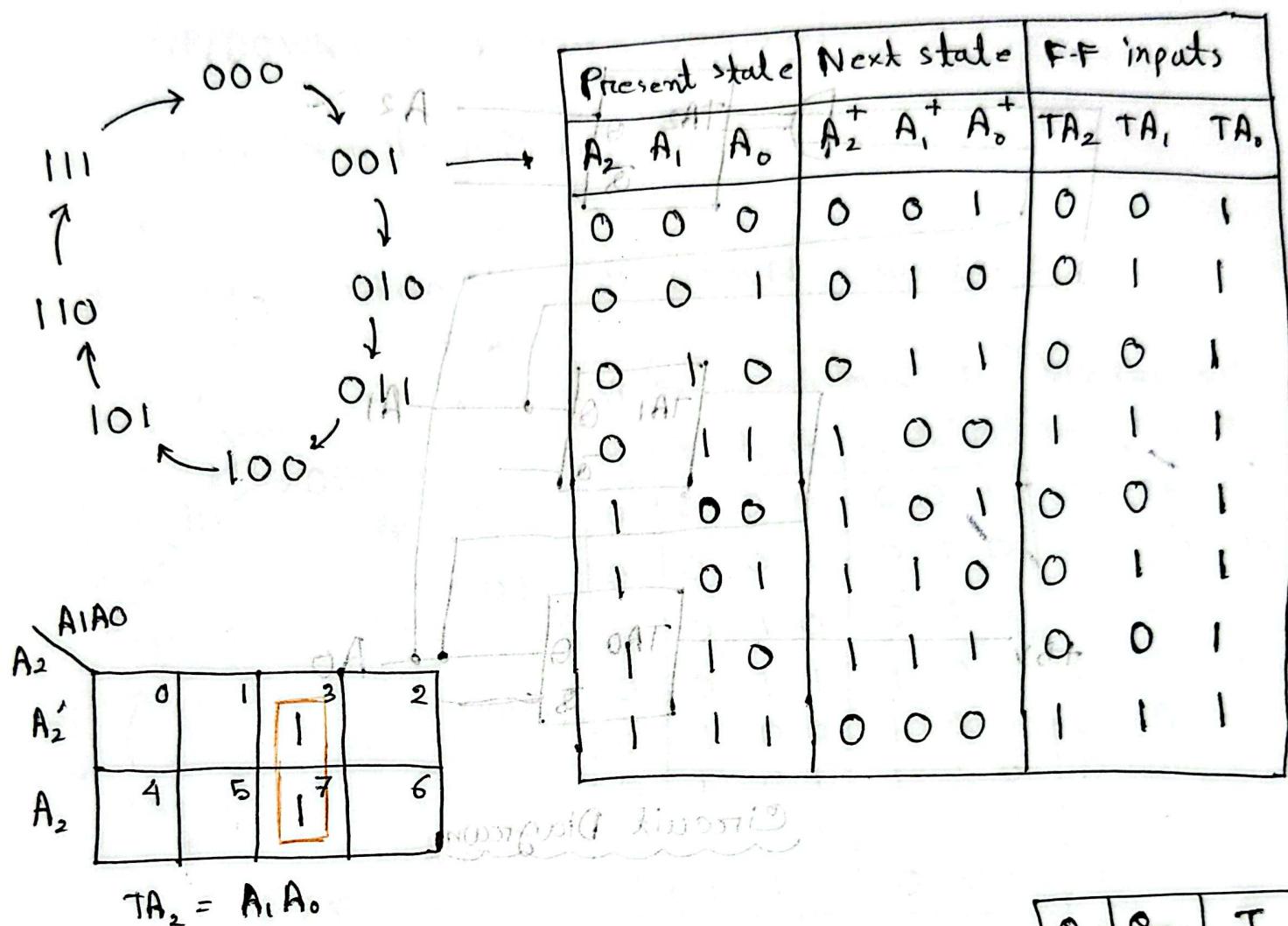
Design a 3-bit synchronous binary UP counter (Using T)



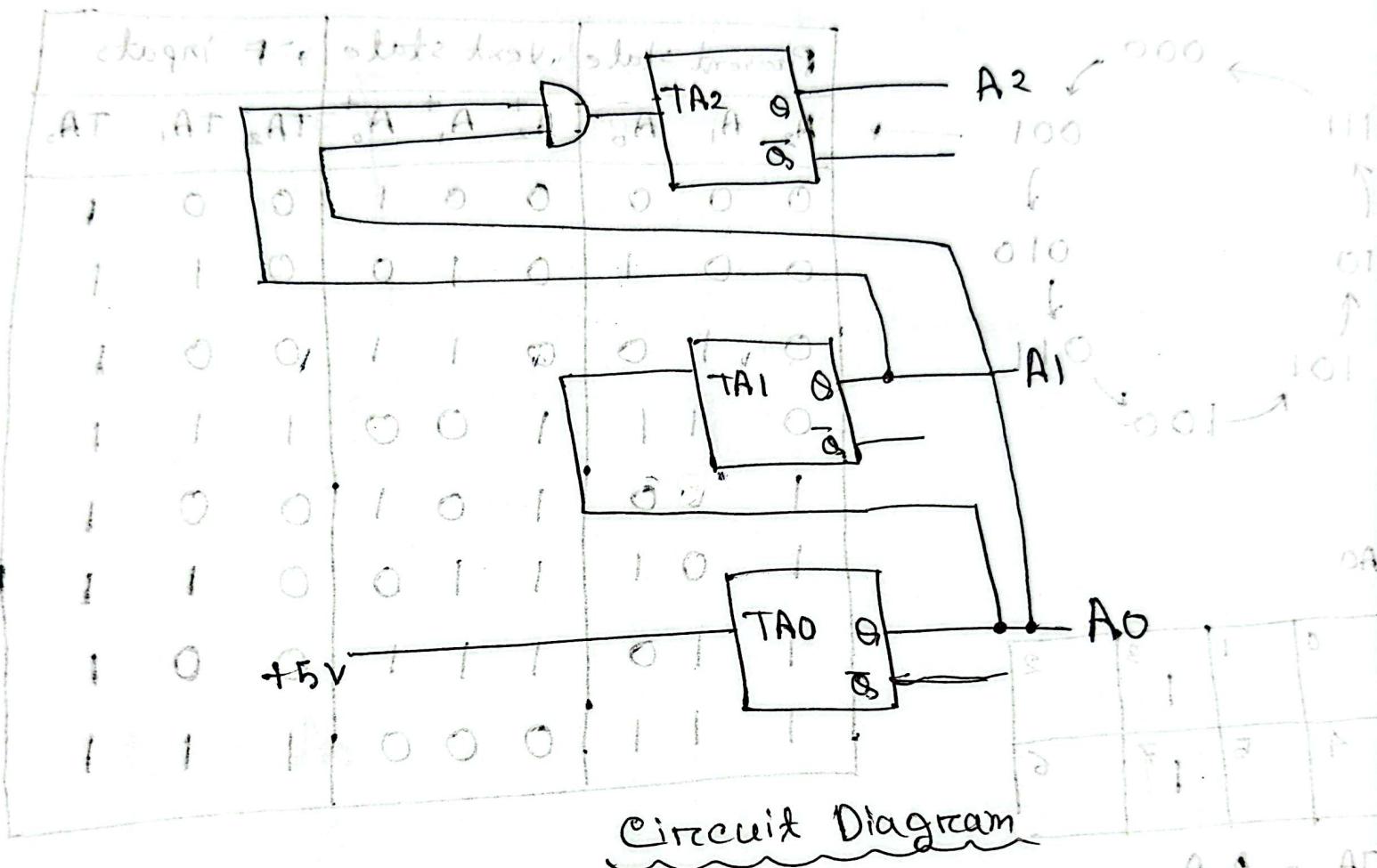station 90 prend en compte les bits de registre  
(T précis)



$$A_1 A_2 = AT$$

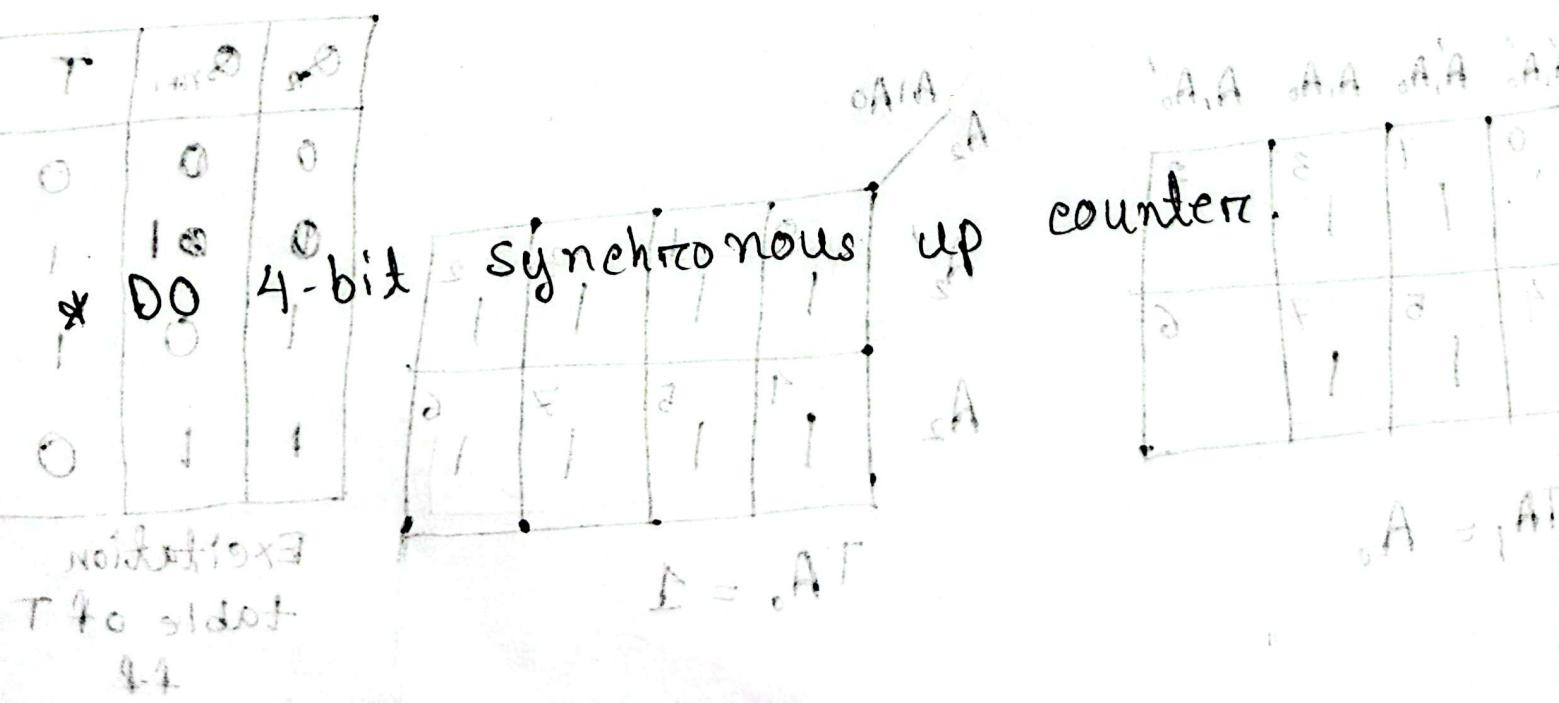


## UP/DOWN synchronous Counters

UP/DOWN = 0 → Count upward

UP/DOWN = 1 → Count downward

\* 3 bit synchronous UP/DOWN Counter:

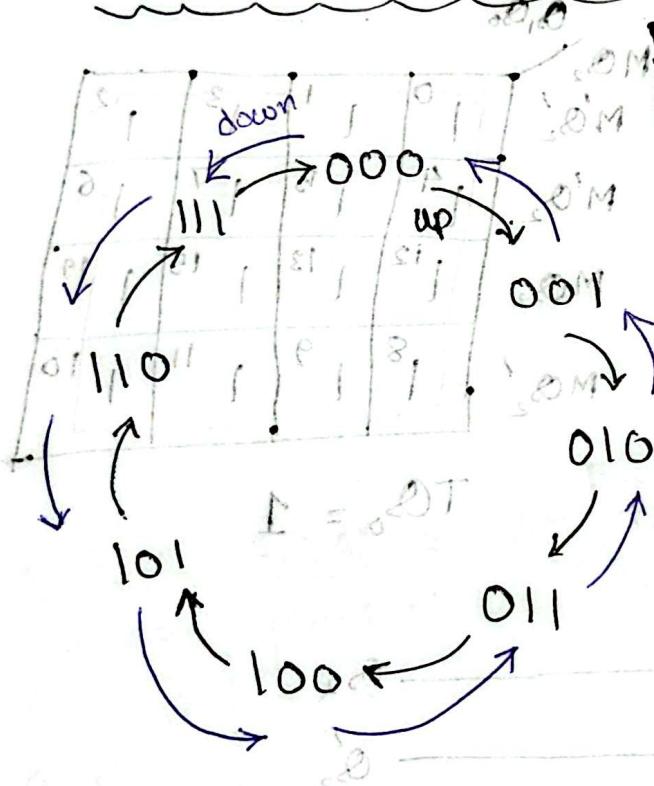

U/D M	Present states			Next states			Flip-Flop inputs		
	$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$TQ_2$	$TQ_1$	$TQ_0$
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	0	1	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	0	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	1	0	0	1	0	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	1	0	1	1	1
1	1	1	1	0	0	0	1	1	1

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

$M'Q_2$	$Q_1Q_2$	$Q_1'Q_2'$	$Q_1Q_3$	$Q_1'Q_3'$	$Q_2Q_3$
$M'Q_2'$	0	1	3	1	2
$M'Q_3$	4	5	7	6	1
$MQ_2$	12	13	15	14	
$MQ_2'$	8	9	11	10	


$M' O_2$	$O, O_0$	$O, O_0'$	$O, O_0$	$O, O_0$	$O, O_0'$						
$M' O_2$	0	1	1	1	3			2			
$M' O_2$	4	1	5	1	7			6			
$M O_2$	12		13		15			14			
$M O_2'$	1							1			
$M O_2'$	8		9		11			10			
$M O_2'$	1							1			

$$TQ_2 = MQ_1 Q_{20} + MQ_1' Q_{20}'$$

$$TQ_1 = M'Q_0 + M_1 Q_0'$$

$M'Q_2$	$O_1Q_2$	$M'Q_2'$	$O_1Q_2'$	$M'Q_2$	$O_1Q_2$
1	0	1	1	3	2
1	4	1	5	1	6
1	12	1	13	1	15
1	8	1	9	1	11
$M'Q_2'$	$O_1Q_2$	$M'Q_2$	$O_1Q_2$	$M'Q_2'$	$O_1Q_2$


$$TO_{S_0} = 1$$

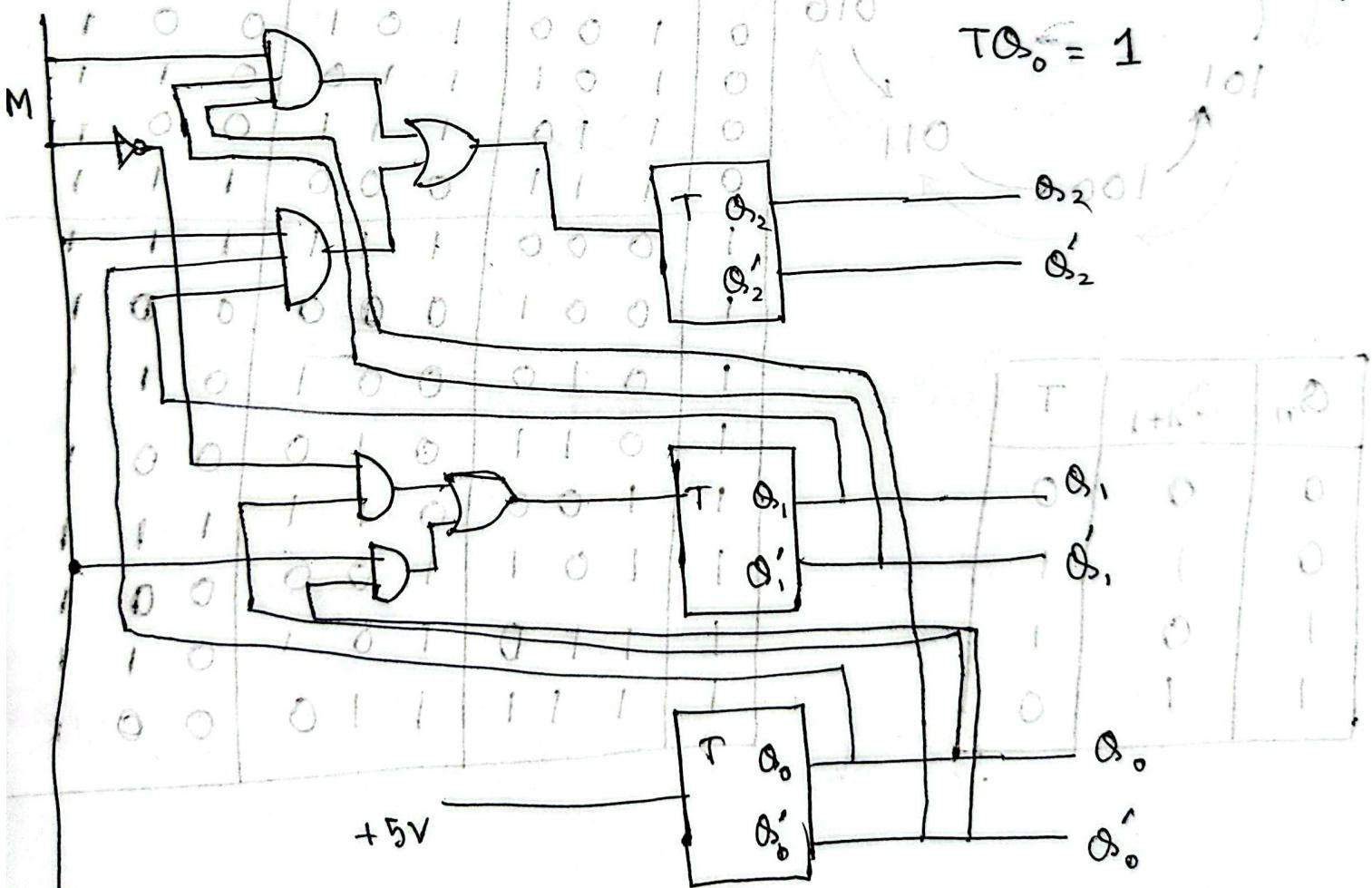
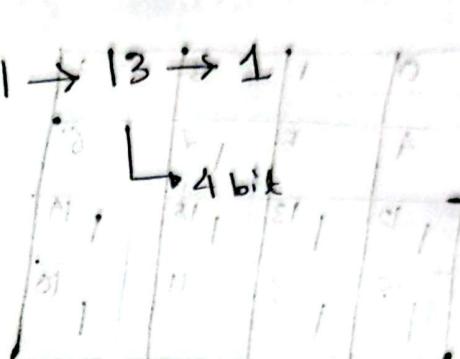
## Circuit Diagram


Implement the following counter using TFF:

$$1 \rightarrow 2 \rightarrow 3 \rightarrow 5 \rightarrow 7 \rightarrow 11 \rightarrow 13 \rightarrow 1$$



$$\text{Q}A_3\text{A}_2\text{A}_1\text{A}_0 + \text{QA}_3\text{A}_2\text{A}_1 + \text{QA}_3\text{A}_2 = 0001$$
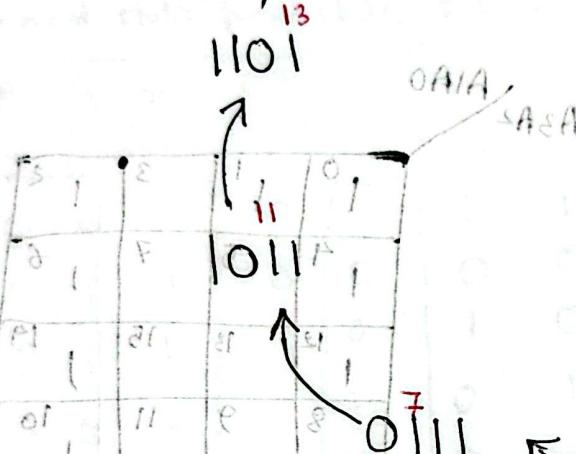
$$\text{Q}A_3\text{A}_2\text{A}_1\text{A}_0 + \text{QA}_3\text{A}_2 + \text{QA}_3\text{A}_1 = 0010$$



$$0010$$

$Q_{n+1}$	$Q_{n+1}$	$SATA$
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table of

Present states	Next states	Flip-flop inputs
0 0 0 0	0 0 0 1	0 0 0 1
0 0 0 1	0 0 1 0	0 0 1 1
0 0 1 0	0 0 1 1	0 0 0 1
0 0 1 1	0 1 0 1	0 1 1 0
0 1 0 0	0 0 0 0	0 0 0 0
0 1 0 1	0 1 1 1	0 0 1 1
0 1 1 0	0 0 0 1	0 1 1 1
0 1 1 1	1 0 1 1	1 0 0 0
1 0 0 0	0 0 0 1	1 0 0 0
1 0 0 1	0 0 0 1	1 0 1 1
1 0 1 0	0 0 0 1	1 0 1 0
1 0 1 1	1 1 0 1	0 1 1 0
1 1 0 0	0 0 0 1	1 1 0 0
1 1 0 1	0 0 0 1	1 1 1 1
1 1 1 0	0 0 0 1	1 1 1 0
1 1 1 1	0 0 0 1	1 1 1 0

For not mentioned state  
use 0001  
(Initial state)

[OR Don't care]  
Use  
XXXX

Truth table for output  $T_{A3}$

$A_3 A_2$	$A_3 A_0$	$T_{A3}$
0 0	0	0
0 1	1	1
1 0	1	1
1 1	0	0

$$T_{A3} = A_3 A_0' + A_3 A_1' + A_2 A_1 A_0$$

$$T_{A2} = A_2 A_0' + A_3 A_2 + A_1 A_0$$

Truth table for output  $T_{A1}$

$A_3 A_2$	$A_3 A_0$	$T_{A1}$
0 0	0	0
0 1	1	1
1 0	0	1
1 1	1	0

Truth table for output  $T_{A0}$

$A_3 A_2$	$A_3 A_0$	$T_{A0}$
0 0	0	0
0 1	1	1
1 0	1	1
1 1	0	0

To didn't violated

$$T_{A1} = A_3' A_1' A_0 + A_3' A_2' A_0$$

$$+ A_2 A_1 A_0' + A_3 A_1$$

for  $T_{A1}$

note: basic then DRAW the Circuit  $\rightarrow$

1000 saw

load

stroke

now load 80

Final


0 0 0 0	0 0 0 0	0 0 0 0	0 0 0 0	0 0 0 0
1 0 0 0	0 1 0 0	0 1 0 0	1 0 0 0	1 0 0 0
0 0 1 0	1 0 0 0	1 0 0 0	0 1 0 0	0 1 0 0
1 0 0 0	0 0 1 0	0 0 1 0	1 1 0 0	1 1 0 0
0 0 0 1	1 0 0 0	1 0 0 0	0 0 1 0	0 0 1 0
1 0 0 0	0 0 0 1	0 0 0 1	1 1 1 0	1 1 1 0
0 0 0 0	1 0 0 0	1 0 0 0	0 1 1 0	0 1 1 0
1 0 0 0	0 1 0 0	0 1 0 0	1 1 0 1	1 1 0 1
0 0 0 0	0 0 1 0	0 0 1 0	0 0 0 1	0 0 0 1
1 0 0 0	0 0 0 1	0 0 0 1	1 0 1 0	1 0 1 0
0 0 0 0	0 0 0 0	0 0 0 0	0 0 0 0	0 0 0 0

(If we need to go in 3 or more states  
we need 2 or more inputs like  $A, B$ )

Implement the following counter using DFF:

Green  $\rightarrow$  Yellow  $\rightarrow$  Red  $\rightarrow$  Yellow  $\rightarrow$  Green.

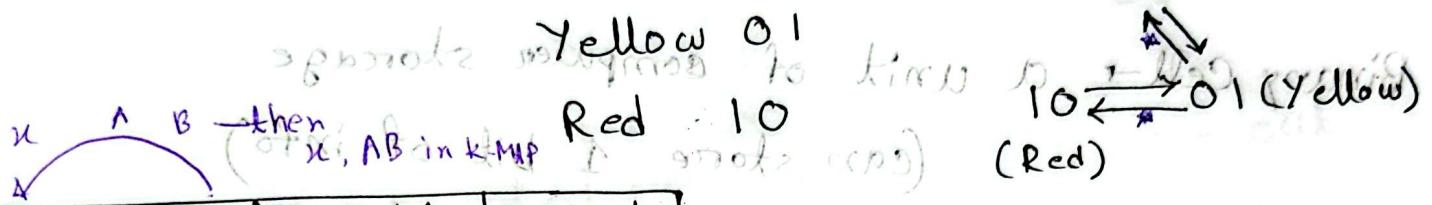Let's assume: Green 00  $\rightarrow$  Yellow 01  $\rightarrow$  Red 10  $\rightarrow$  Yellow 01  $\rightarrow$  Green 00



Present states			Next states		F-F inputs	
A	B	x	$A + B'$	$D$	A	B
0	0	0	0	1	0	1
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	1	0	1	1
1	0	0	0	1	0	1
1	0	1	1	0	1	1
1	1	0	X	X	X	X
1	1	1	X	X	X	X

Excitation table of D-FF

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

We have used don't care since  $A = X$


$Bx B'x' B'x Bx Bx'$		$Bx B'x' B'x Bx Bx'$	
$A'$	$A$	$A'$	$A$
0	1	1	2
4	5	X	6

$Bx B'x' B'x Bx Bx'$		$Bx B'x' B'x Bx Bx'$	
$A'$	$A$	$A'$	$A$
0	1	3	2
4	5	X	6

$$DA = Bx$$

$$DB = B'$$

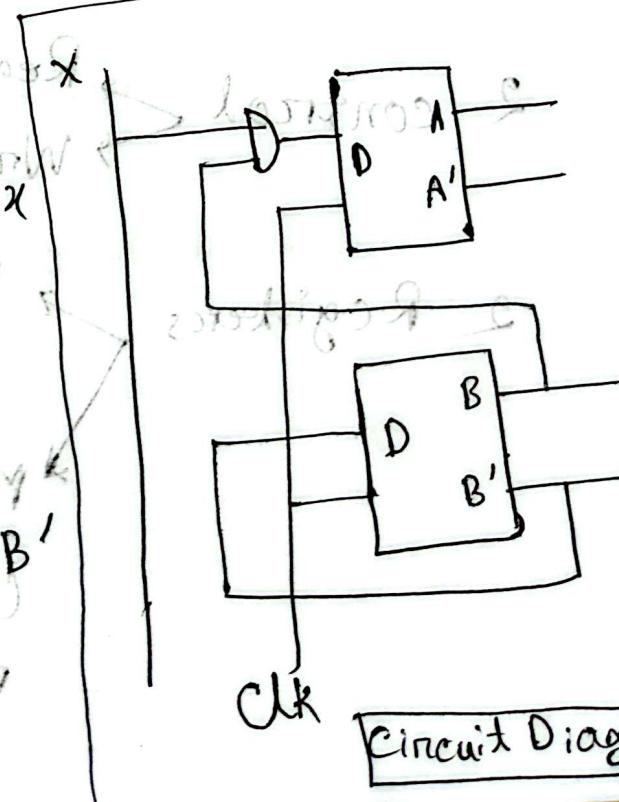

Circuit Diagram